
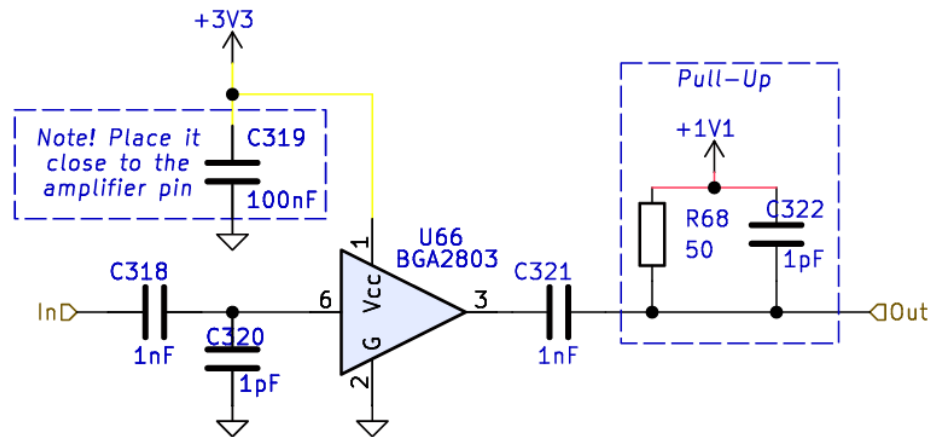


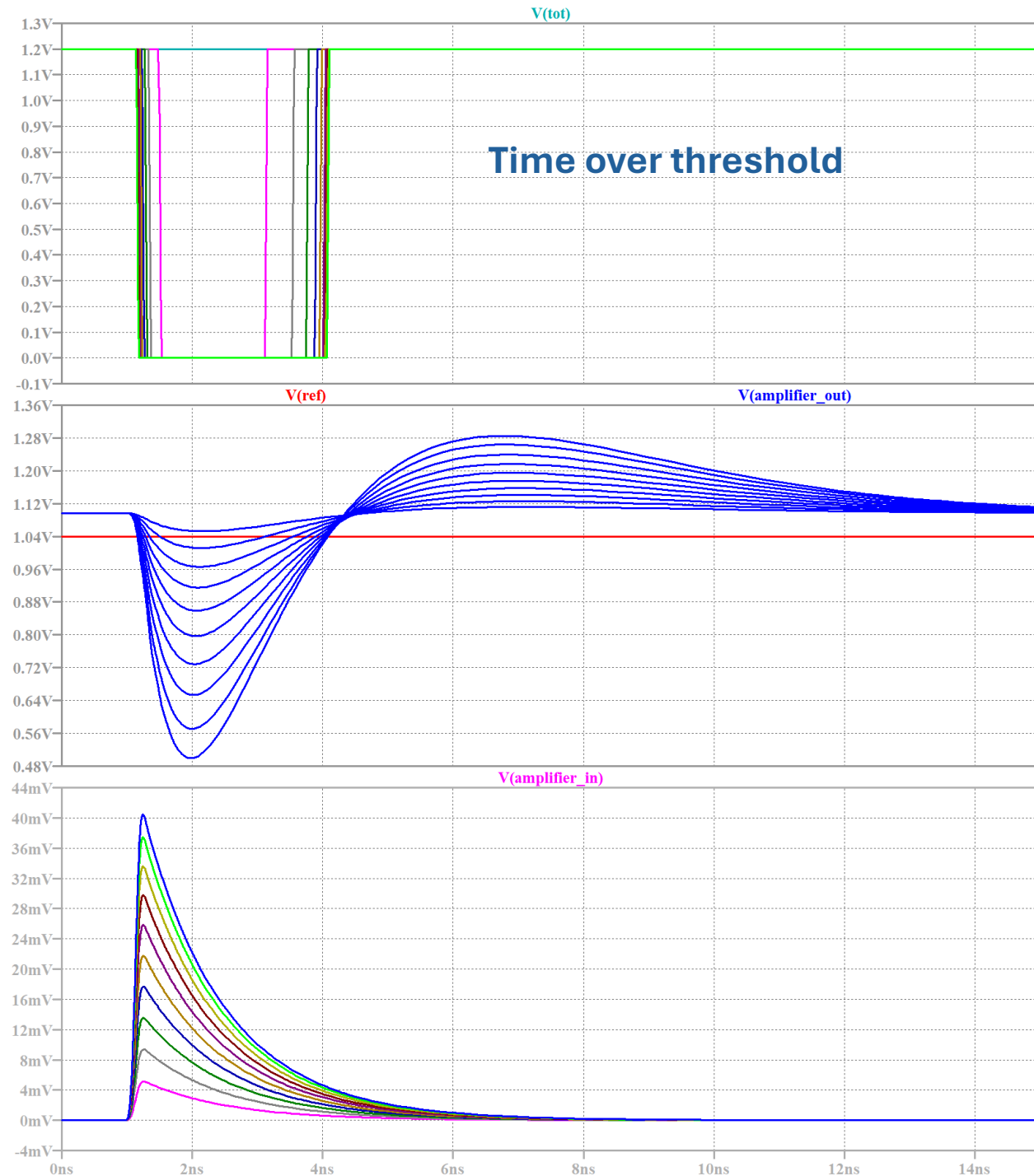
New Amplifier Based on BGA2803 RF block – SPICE sim for 1 Ch



- page_4: <https://jspc29.x-matter.uni-frankfurt.de/trb/schematics/PADIWA3-all.pdf>
- W. Zhi et al 2024 JINST 19 P06011 DOI 10.1088/1748-0221/19/06/P06011
- Joshua W Cates et al 2018 Phys. Med. Biol. 63 185022 DOI 10.1088/1361-6560/aadbcd
- F. Simon NIM-A Volume 926, 11 May 2019, Pages 85-100 Doi.org/10.1016/j.nima.2018.11.042




New Amplifier Based on BGA2803 RF block

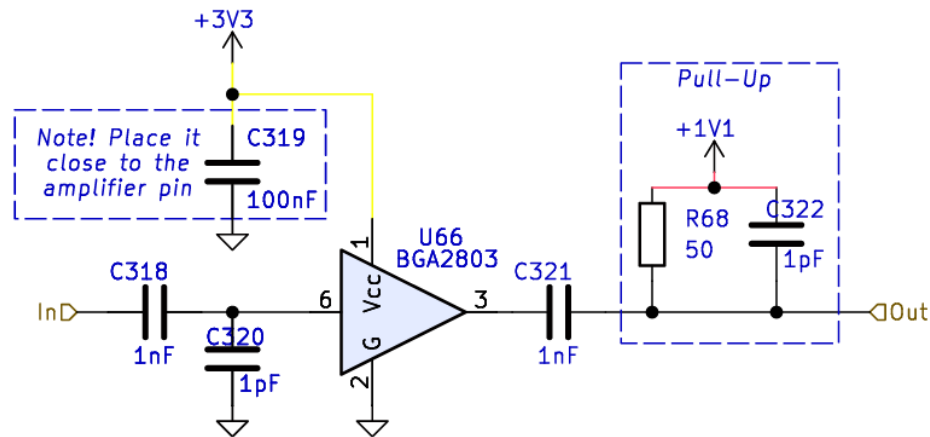


Hamamatsu S13552
https://www.hamamatsu.com/eu/en/product/optical-sensors/mppc/mppc_mppc-array/S13552.html

TOP VIEW

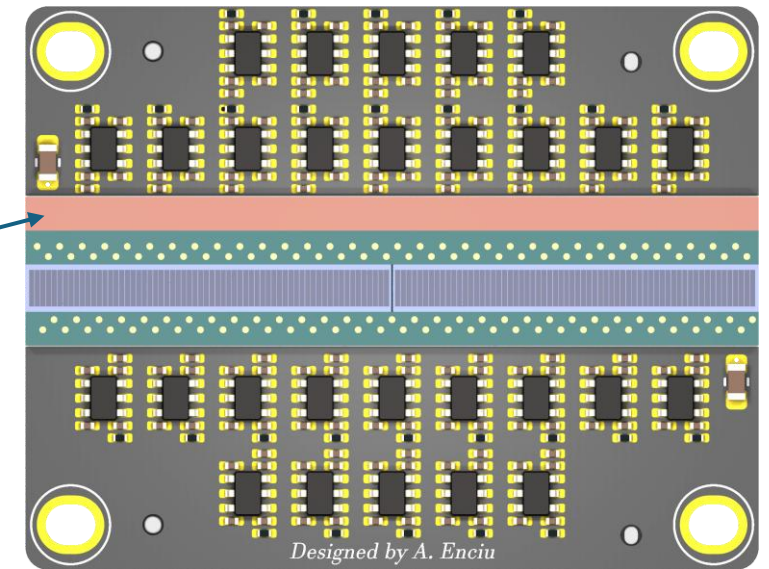



BOTTOM VIEW

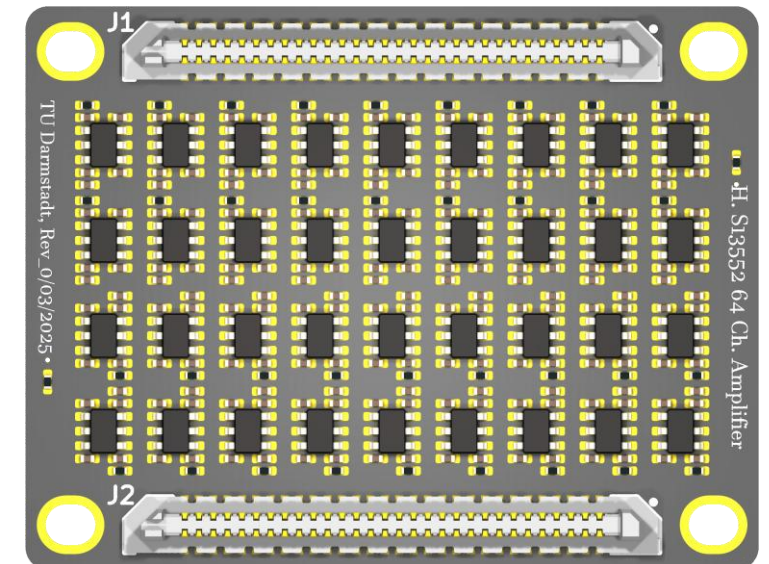



- page_4: <https://jpsc29.x-matter.uni-frankfurt.de/trb/schematics/PADIWA3-all.pdf>
- W. Zhi et al 2024 JINST 19 P06011 DOI 10.1088/1748-0221/19/06/P06011
- Joshua W Cates et al 2018 Phys. Med. Biol. 63 185022 DOI 10.1088/1361-6560/aadbcd
- F. Simon NIM-A Volume 926, 11 May 2019, Pages 85-100 Doi.org/10.1016/j.nima.2018.11.042

BGA2803 Demo Board

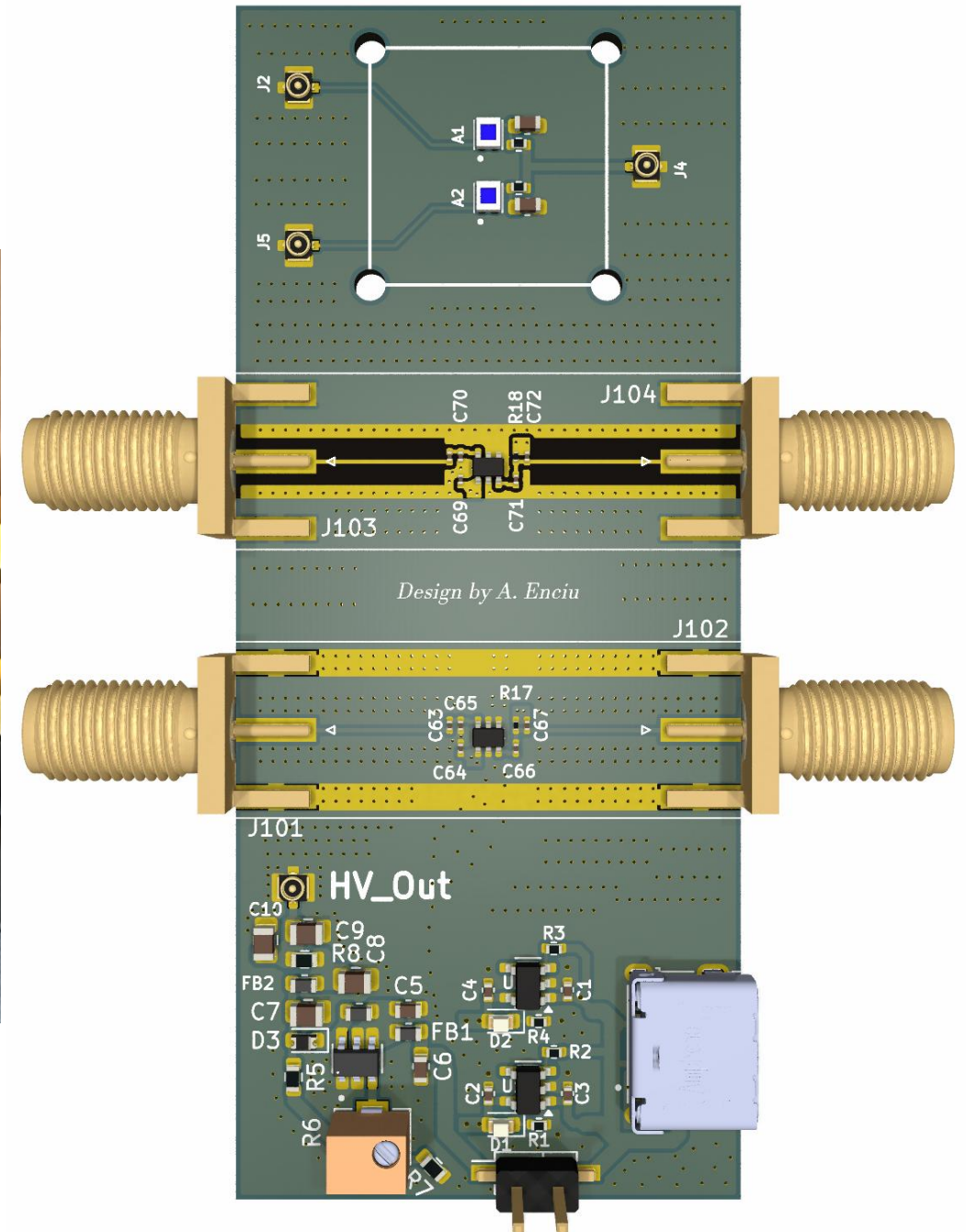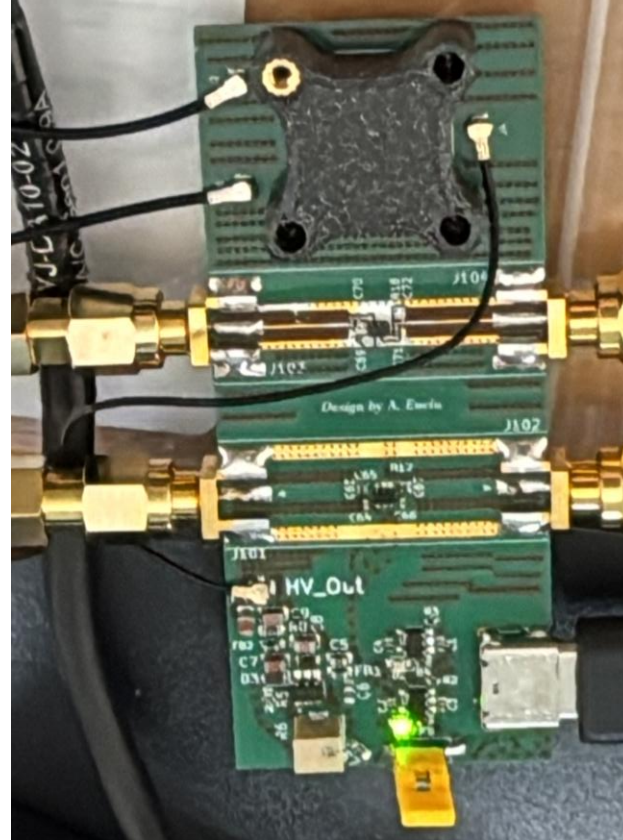- 2 RF amplifiers
- 2 SiPMs
- 1 HV PSU
- Power via USB-C





Cosmics on the oscilloscope

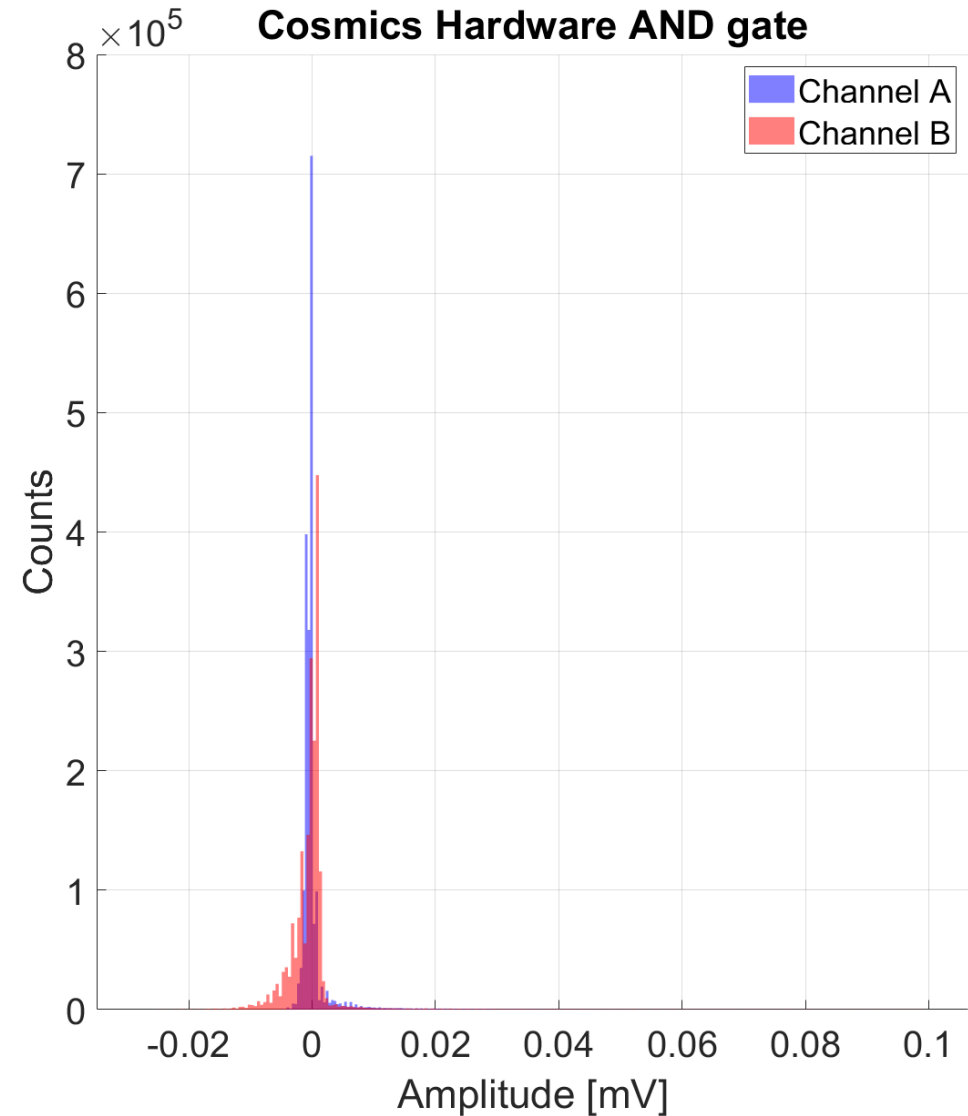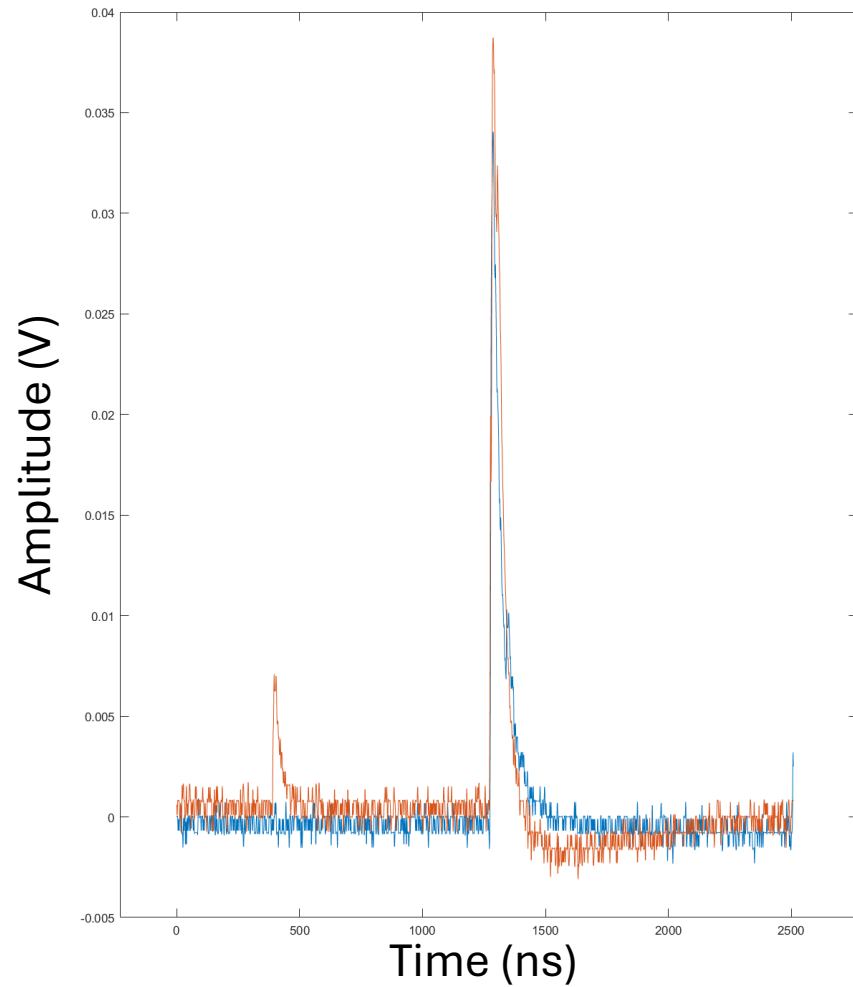

64-Ch FPGA-Based MCA

Prototype (1-Ch) CMOD-S7/A7

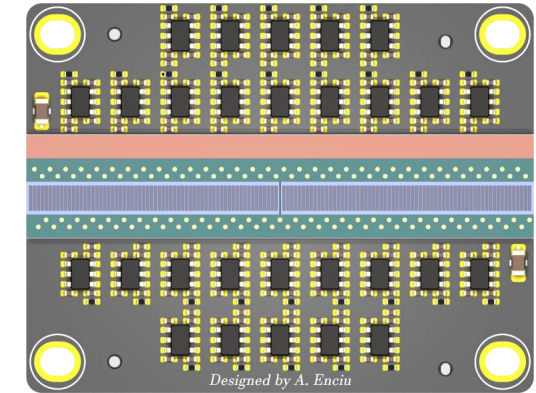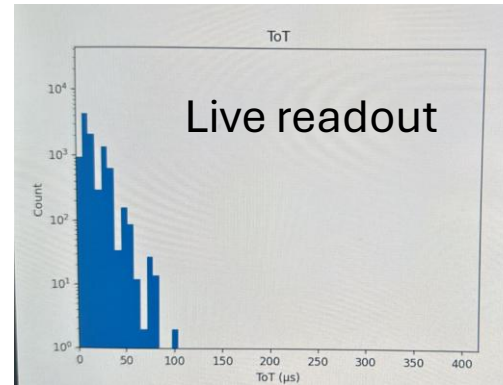- 12 MHz Clock (83.33 ns/cycle)
- 16-bit counter (83.33 ns – 5.4 ms)
- Data transmitted via USB 2.0



Prototype (64-Ch) Alinx 7103

- 100 MHz clock (10 ns/cycle)
- Data transmitted via UDP

Custom made FPGA Board

- **Alinx board specs in a smaller format**

